

# Homework 3

Michael Brodskiy

Professor: A. Abur

October 22, 2024

## Chapter 9:

1. Per the connection/disconnection rules of  $Y_{bus}$ , we know that adding a connection between 2 and 4 will result only in changes to  $Y_{22}$ ,  $Y_{24}$ ,  $Y_{42}$ , and  $Y_{44}$ . Thus, we may rewrite all other values from the matrix obtained in Example 9.4:

$$Y_{bus} = \begin{bmatrix} 1.4 - j18.66 & -1.4 + j18.66 & 0 & 0 & 0 \\ -1.4 + j18.66 & ??? & -.318 + j3.98 & ??? & 0 \\ 0 & -.318 + j3.98 & .636 - j7.73 & -.318 + j3.98 & 0 \\ 0 & ??? & -.318 + j3.98 & ??? & -.932 + j12.43 \\ 0 & 0 & 0 & -.932 + j12.43 & .932 - j12.43 \end{bmatrix}$$

Per our connection rules, connecting a line from terminal 2 to terminal 4 results in addition of the new admittance to diagonal entries:

$$Y'_{22} = Y_{22} + (.01 + .15j)^{-1} + .11j$$

$$Y'_{44} = Y_{44} + (.01 + .15j)^{-1} + .11j$$

This gives us:

$$Y'_{22} = (2.16 - 29.104j) + (.01 + .15j)^{-1} + .11j$$

$$Y'_{44} = (1.692 - 22.877j) + (.01 + .15j)^{-1} + .11j$$

And finally:

$$Y'_{22} = 2.6025 - 35.6312j[p.u.]$$

$$Y'_{44} = 2.1345 - 29.4042j[p.u.]$$

We then find the equivalent admittance by taking the inverse of the impedance:

$$Z_{eq} = \frac{(.01 + .15j)^2}{2(.01 + .15j)}$$

$$Y_{eq} = \frac{2(.01 + .15j)}{(.01 + .15j)^2}$$

$$Y_{eq} = \frac{2}{(.01 + .15j)}$$

$$Y_{24} = Y_{42} = -Y_{eq} = -.885 + 13.2743j[p.u.]$$

This allows us to construct the modified matrix as:

$$Y_{bus} = \begin{bmatrix} 1.4 - j18.66 & -1.4 + j18.66 & 0 & 0 & 0 \\ -1.4 + j18.66 & 2.6025 - 35.6312j & -.318 + j3.98 & -.885 + 13.2743j & 0 \\ 0 & -.318 + j3.98 & .636 - j7.73 & -.318 + j3.98 & 0 \\ 0 & -.885 + 13.2743j & -.318 + j3.98 & 2.1345 - 29.4042j & -.932 + j12.43 \\ 0 & 0 & 0 & -.932 + j12.43 & .932 - j12.43 \end{bmatrix}$$

2. We can expand the given table to write:

| From-To | Reactance [p.u.] | Admittance [pu] |
|---------|------------------|-----------------|
| 1-2     | .04j             | -25j            |
| 1-6     | .06j             | -16.667j        |
| 2-4     | .03j             | -33.333j        |
| 2-3     | .02j             | -50j            |
| 3-4     | .08j             | -12.5j          |
| 4-5     | .06j             | -16.667j        |
| 5-6     | .05j             | -20j            |

This allows us to write the corresponding connections into the matrix:

$$Y_{bus} = \begin{bmatrix} & 25 & & & & 16.667 \\ 25 & & 50 & 33.333 & & \\ & 50 & & 12.5 & & \\ & 33.333 & 12.5 & & 16.667 & \\ & & & 16.667 & & 20 \\ 16.667 & & & & 20 & \end{bmatrix} j$$

By observation from the diagram, we may write all of the following admittances as zero:

| From | To    |
|------|-------|
| 1    | 3,4,5 |
| 2    | 5,6   |
| 3    | 1,5,6 |
| 4    | 1,6   |
| 5    | 1,2,3 |
| 6    | 2,3,4 |

This gives us:

$$Y_{bus} = \begin{bmatrix} & 25 & 0 & 0 & 0 & 16.667 \\ 25 & & 50 & 33.333 & 0 & 0 \\ 0 & 50 & & 12.5 & 0 & 0 \\ 0 & 33.333 & 12.5 & & 16.667 & 0 \\ 0 & 0 & 0 & 16.667 & & 20 \\ 16.667 & 0 & 0 & 0 & 20 & \end{bmatrix} j$$

We see that now only the diagonal is left. Thus, we write KVL equations whilst imagining a current element  $I_n$  for each bus  $n$ . This allows us to write:

$$\begin{aligned} I_1 &= (V_1 - V_2)(-25j) + (V_1 - V_6)(-16.667j) \\ I_2 &= (V_2 - V_1)(-25j) + (V_2 - V_3)(-50j) + (V_2 - V_4)(-33.333j) \\ I_3 &= (V_3 - V_2)(-50j) + (V_3 - V_4)(-12.5j) \\ I_4 &= (V_4 - V_2)(-33.333j) + (V_4 - V_3)(-12.5j) + (V_4 - V_5)(-16.667j) \\ I_5 &= (V_5 - V_4)(-16.667j) + (V_5 - V_6)(-20j) \\ I_6 &= (V_6 - V_1)(-16.667j) + (V_6 - V_5)(-20j) \end{aligned}$$

Simplifying the equations, we obtain

$$\begin{aligned} I_1 &= j[-41.667V_1 + 25V_2 + 16.667V_6] \\ I_2 &= j[-108.33V_2 + 25V_1 + 50V_3 + 33.333V_4] \\ I_3 &= j[-62.5V_3 + 50V_2 + 12.5V_4] \\ I_4 &= j[-62.5V_4 + 33.333V_2 + 12.5V_3 + 16.667V_5] \\ I_5 &= j[-36.667V_5 + 16.667V_4 + 20V_6] \\ I_6 &= j[-36.667V_6 + 16.667V_1 + 20V_5] \end{aligned}$$

Given that we know:

$$I_n = Y_{bus}V_n$$

We look at the coefficients from the currents to obtain the diagonals:

$$Y_{bus} = \begin{bmatrix} -41.667 & 25 & 0 & 0 & 0 & 16.667 \\ 25 & -108.33 & 50 & 33.333 & 0 & 0 \\ 0 & 50 & -62.5 & 12.5 & 0 & 0 \\ 0 & 33.333 & 12.5 & -62.5 & 16.667 & 0 \\ 0 & 0 & 0 & 16.667 & -36.667 & 20 \\ 16.667 & 0 & 0 & 0 & 20 & -36.667 \end{bmatrix} j[p.u.]$$

3. Adding another connection between buses 1 and 5 would mean that only the  $nm$ -th elements are modified, with  $nm$  being any combination of 1 and 5. Thus, we see that, with this  $-10j$  admittance, we get two new terms at 15 and 51:

$$Y_{bus} = \begin{bmatrix} ? & 25 & 0 & 0 & 10 & 16.667 \\ 25 & -108.33 & 50 & 33.333 & 0 & 0 \\ 0 & 50 & -62.5 & 12.5 & 0 & 0 \\ 0 & 33.333 & 12.5 & -62.5 & 16.667 & 0 \\ 10 & 0 & 0 & 16.667 & ? & 20 \\ 16.667 & 0 & 0 & 0 & 20 & -36.667 \end{bmatrix} j$$

We then re-check the current equations for buses 1 and 5:

$$I_1 = j[-51.667V_1 + 25V_2 + 10V_5 + 16.667V_6]$$

$$I_5 = j[-46.667V_5 + 10V_1 + 16.667V_4 + 20V_6]$$

Thus, we get:

$$Y_{bus} = \begin{bmatrix} -51.667 & 25 & 0 & 0 & 10 & 16.667 \\ 25 & -108.33 & 50 & 33.333 & 0 & 0 \\ 0 & 50 & -62.5 & 12.5 & 0 & 0 \\ 0 & 33.333 & 12.5 & -62.5 & 16.667 & 0 \\ 10 & 0 & 0 & 16.667 & -46.667 & 20 \\ 16.667 & 0 & 0 & 0 & 20 & -36.667 \end{bmatrix} j[p.u.]$$

4. We may begin finding diagonal entries by summing all of the admittances incident at each bus:

$$Y_{11} = \frac{1}{.2j} + \frac{1}{.25j} + \frac{.24j}{2} + \frac{.3j}{2}$$

$$Y_{22} = \frac{1}{.2j} + \frac{1}{.1j} + \frac{.24j}{2} + \frac{.16j}{2} + .3j$$

$$Y_{33} = \frac{1}{.25j} + \frac{1}{.1j} + \frac{.16j}{2} + \frac{.3j}{2} - .6j$$

Solving, we get:

$$\begin{aligned}Y_{11} &= -5j - 4j + .12j + .15j \\Y_{22} &= -5j - 10j + .12j + .08j + .3j \\Y_{33} &= -4j - 10j + .08j + .15j - .6j\end{aligned}$$

And finally:

$$\begin{aligned}Y_{11} &= -8.73j[p.u.] \\Y_{22} &= -14.5j[p.u.] \\Y_{33} &= -14.37j[p.u.]\end{aligned}$$

- (a) The off-diagonal elements will simply be the admittances of the connections, which gives us:

$$Y_{bus} = \begin{bmatrix} -8.73 & 5 & 4 \\ 5 & -14.5 & 10 \\ 4 & 10 & -14.37 \end{bmatrix} j$$

- (b) With bus 2 gone, we may write:

$$\begin{aligned}Y_{11} &= -4j + \frac{.3j}{2} \\Y_{33} &= -4j + \frac{.3j}{2} - .6j\end{aligned}$$

And then:

$$\begin{aligned}Y_{11} &= -3.85j \\Y_{33} &= -4.45j\end{aligned}$$

The off-diagonal terms are then simply 4j:

$$Y_{bus} = \begin{bmatrix} -3.85 & 4 \\ 4 & -4.45 \end{bmatrix} j$$

5. We write KCL equations which integrate the new voltage source (note the currents  $I_2$  and  $I_3$  are zero, but this is not reflected below to simplify further analysis):

$$\begin{aligned}I_1 &= V_1(-.8696j) + (V_1 - V_2)(-5j) + .12V_1j + (V_1 - V_3)(-4j) + .15V_1j \\I_2 &= (V_2)(.3j) + (V_2 - V_1)(-5j) + .12V_2j + (V_2 - V_3)(-10j) + .08V_2j \\I_3 &= (V_3)(-.6j) + (V_3 - V_1)(-4j) + .15V_3j + (V_3 - V_2)(-10j) + .08V_3j\end{aligned}$$

This gives us:

$$[-9.5396V_1 + 5V_2 + 4V_3]j = I_1$$

$$[-14.5V_2 + 5V_1 + 10V_3]j = I_2$$

$$[-14.37V_3 + 4V_1 + 10V_2]j = I_3$$

From which we may build:

$$Y_{bus} = \left( \begin{bmatrix} -9.5396 & 5 & 4 \\ 5 & -14.5 & 10 \\ 4 & 10 & -14.37 \end{bmatrix} j \right) [p.u.]$$