

Lecture 2

Michael Brodskiy

Professor: A. Ali

September 12, 2024

- Capacitors may be connected in parallel to increase power factor
- For a balanced three-phase circuit, we may analyze each phase independently
- Connections may be in 'Y' or Delta form; for analysis, we prefer 'Y'
- To convert from Delta-type connections, we may use the following:

- Impedances:

$$Z_Y = \frac{1}{3}Z_\Delta$$

- Sources:

$$\hat{V}_{LL} = \sqrt{3}\hat{V}_{LN}e^{j30^\circ}$$

- To use these analyses methods, we must assume:
 - The system is 3-phased and balanced
 - All the loads and sources are 'Y'-connected
 - No mutual inductance between phases
- This then allows us to assume:
 - All the neutrals will be acting at the same potential
 - Phases will be completely decoupled
 - All network variables occur in balanced sets of the same sequence as the sources