

Lab Five
Power Systems Analysis
EECE5682

Michael BRODSKIY
Brodskiy.M@Northeastern.edu

November 12, 2024

Date Performed: November 12, 2024
Instructor: Professor ABUR

Abstract

This laboratory experiment orients the performer with the Power Education Toolbox (PET) program. Furthermore, the experiment solidifies concepts related to bus-based systems, including power flow solutions, generation of an admittance matrix, and the affects of connecting/disconnecting components.

KEYWORDS: PET, bus, power flow, admittance matrix

1 Introduction & Objectives

We begin by constructing the provided 5-bus system in the Power Education Toolbox (PET) program. The system looks as follows:

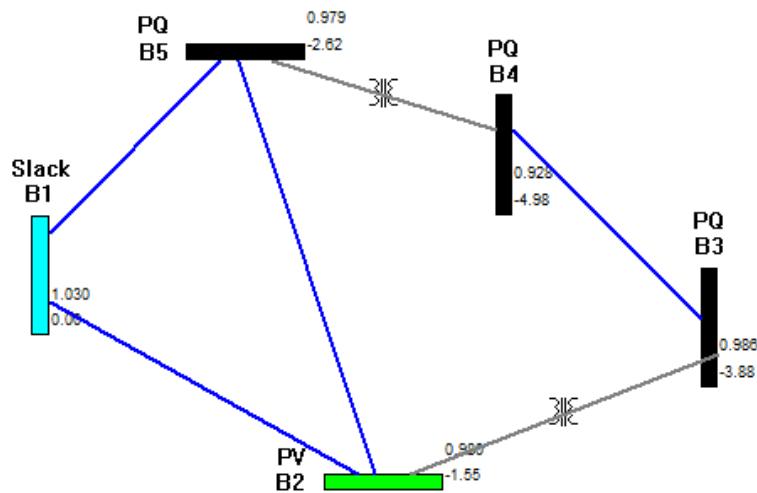


Figure 1: The Five-Bus System

2 Results

The Results shown in Parts (1-4) are obtained from the data files generated by PET.

2.1 Part 1

CONVERGENCE SUMMARY						
ITER		DELP		DELO		
0.0		0.960294				
0.5				1.009047		
1.0		0.174055				
1.5				0.024444		
2.0		0.011893				
2.5				0.001464		
3.0		0.001561				
3.5				0.000081		
4.0		0.000109				
***** POWER FLOW REPORT *****						
BUS NO.	VOLTAGE (PU)	ANGLE (DEG)	GENERATION (MW) (MVAR)		LOAD (MW) (MVAR)	
1	1.0300	0.00	139.99496	50.81974	0.00000	0.00000
T0-BUS	5	71.81894	MW	8.27556	MVAR	
T0-BUS	2	68.17602	MW	42.54447	MVAR	
2	0.9800	-1.60	135.00000	42.64991	75.00000	60.00000
T0-BUS	5	40.35718	MW	-26.90932	MVAR	
T0-BUS	3	86.18706	MW	87.60418	MVAR	
T0-BUS	1	-66.53333	MW	-78.04241	MVAR	
3	1.0249	-3.86	0.00000	0.00000	60.00000	50.00000
T0-BUS	4	26.18853	MW	30.94921	MVAR	
T0-BUS	2	-86.18706	MW	-80.94917	MVAR	
4	0.9439	-4.80	0.00000	0.00000	70.00000	55.00000
T0-BUS	5	-45.17653	MW	0.97466	MVAR	
T0-BUS	3	-24.82372	MW	-55.97490	MVAR	
5	0.9831	-2.66	0.00000	0.00000	65.00000	45.00000
T0-BUS	1	-70.01796	MW	-54.15830	MVAR	
T0-BUS	2	-40.15642	MW	8.44325	MVAR	
T0-BUS	4	45.17653	MW	0.71506	MVAR	

Figure 2: Power Flow — Part 1

1	1	(9.109589,	-25.508904)
2	2	(10.882353,	-61.858901)
3	3	(2.000000,	-25.850000)
4	4	(2.000000,	-19.413368)
5	5	(9.991942,	-46.638316)
5	1	(-4.109589,	10.958904)
1	5	(-4.109589,	10.958904)
2	1	(-5.000000,	15.000000)
1	2	(-5.000000,	15.000000)
5	2	(-5.882353,	23.529412)
2	5	(-5.882353,	23.529412)
4	3	(-2.000000,	6.000000)
3	4	(-2.000000,	6.000000)
5	4	(0.000000,	13.020833)
4	5	(0.000000,	13.020833)
3	2	(0.000000,	21.739130)
2	3	(0.000000,	21.739130)

Figure 3: Y_{Bus} — Part 1

2.2 Part 2

CONVERGENCE SUMMARY						
ITER		DEL P		DEL Q		
0.0		0.960294				
0.5				1.009047		
1.0		0.174055				
1.5				0.024444		
2.0		0.011893				
2.5				0.001464		
3.0		0.001561				
3.5				0.026499		
4.0		0.009876				
4.5				0.001969		
5.0		0.000252				
5.5				0.000105		
***** POWER FLOW REPORT *****						
BUS NO.	VOLTAGE (PU)	ANGLE (DEG)	GENERATION (MW)		LOAD (MW)	
				(MVAR)		(MVAR)
1	1.0300	0.00	140.13101	53.89642	0.00000	0.00000
T0-BUS	5		71.87868 MW	9.36384 MVAR		
T0-BUS	2		68.20592 MW	44.53257 MVAR		
2	0.9788	-1.58	135.00000	40.00000	75.00000	60.00000
T0-BUS	5		40.34643 MW	-27.60321 MVAR		
T0-BUS	3		86.16390 MW	87.43051 MVAR		
T0-BUS	1		-66.51393 MW	-79.83661 MVAR		
3	1.0237	-3.85	0.00000	0.00000	60.00000	50.00000
T0-BUS	4		26.16471 MW	30.77342 MVAR		
T0-BUS	2		-86.16390 MW	-80.77473 MVAR		
4	0.9429	-4.80	0.00000	0.00000	70.00000	55.00000
T0-BUS	5		-45.19308 MW	0.75512 MVAR		
T0-BUS	3		-24.80669 MW	-55.75271 MVAR		
5	0.9822	-2.65	0.00000	0.00000	65.00000	45.00000
T0-BUS	1		-70.05352 MW	-55.13915 MVAR		
T0-BUS	2		-40.14263 MW	9.18945 MVAR		
T0-BUS	4		45.19308 MW	0.93917 MVAR		

Figure 4: Power Flow — Part 2

1	1	(9.109589,	-25.508904)
2	2	(10.882353,	-61.858901)
3	3	(2.000000,	-25.850000)
4	4	(2.000000,	-19.413368)
5	5	(9.991942,	-46.638316)
5	1	(-4.109589,	10.958904)
1	5	(-4.109589,	10.958904)
2	1	(-5.000000,	15.000000)
1	2	(-5.000000,	15.000000)
5	2	(-5.882353,	23.529412)
2	5	(-5.882353,	23.529412)
4	3	(-2.000000,	6.000000)
3	4	(-2.000000,	6.000000)
5	4	(0.000000,	13.020833)
4	5	(0.000000,	13.020833)
3	2	(0.000000,	21.739130)
2	3	(0.000000,	21.739130)

Figure 5: Y_{Bus} — Part 2

2.3 Part 3

CONVERGENCE SUMMARY						
ITER		DELP		DELQ		
0.0		0.960294		1.189175		
0.5						
1.0		0.176448				
1.5				0.024831		
2.0		0.011840				
2.5				0.001362		
3.0		0.001713				
3.5				0.000098		
4.0		0.000119				
***** POWER FLOW REPORT *****						
BUS NO.	VOLTAGE (PU)	ANGLE (DEG)	GENERATION (MW)		LOAD (MW)	
				(MVAR)		(MVAR)
1	1.0300	0.00	140.14602	49.48200	0.00000	0.00000
TO-BUS	5	71.65923	MW	7.03298	MVAR	
TO-BUS	2	68.48679	MW	42.45046	MVAR	
2	0.9800	-1.61	135.00000	21.33284	75.00000	60.00000
TO-BUS	5	39.78992	MW	-29.27043	MVAR	
TO-BUS	3	87.06034	MW	68.53895	MVAR	
TO-BUS	1	-66.83836	MW	-77.93116	MVAR	
3	1.0339	-3.88	0.00000	0.00000	60.00000	50.00000
TO-BUS	4	27.06192	MW	34.50617	MVAR	
TO-BUS	2	-87.06034	MW	-63.12906	MVAR	
4	0.9476	-4.77	0.00000	0.00000	70.00000	55.00000
TO-BUS	5	-44.47562	MW	4.39449	MVAR	
TO-BUS	3	-25.52451	MW	-59.39468	MVAR	
5	0.9841	-2.67	0.00000	0.00000	65.00000	45.00000
TO-BUS	1	-69.88875	MW	-53.04729	MVAR	
TO-BUS	2	-39.58479	MW	10.80168	MVAR	
TO-BUS	4	44.47562	MW	-2.75433	MVAR	

Figure 6: Power Flow — Part 3

1	1	(9.109589,	-25.508904)
2	2	(10.882353,	-61.858901)
3	3	(2.000000,	-25.650000)
4	4	(2.000000,	-19.413368)
5	5	(9.991942,	-46.638316)
5	1	(-4.109589,	10.958904)
1	5	(-4.109589,	10.958904)
2	1	(-5.000000,	15.000000)
1	2	(-5.000000,	15.000000)
5	2	(-5.882353,	23.529412)
2	5	(-5.882353,	23.529412)
4	3	(-2.000000,	6.000000)
3	4	(-2.000000,	6.000000)
5	4	(0.000000,	13.020833)
4	5	(0.000000,	13.020833)
3	2	(0.000000,	21.739130)
2	3	(0.000000,	21.739130)

Figure 7: Y_{Bus} — Part 3

2.4 Part 4

CONVERGENCE SUMMARY						
ITER		DELQ		DELQ		
0.0		0.960294		1.097912		
0.5						
1.0		0.163774		0.043224		
1.5						
2.0		0.020720		0.005107		
2.5						
3.0		0.000910				
3.5				0.000382		
***** POWER FLOW REPORT *****						
BUS NO.	VOLTAGE (PU)	ANGLE (DEG)	GENERATION (MW)	(MVAR)	LOAD (MW)	(MVAR)
1	1.0300	0.00	139.31754	64.25957	0.00000	0.00000
T0-BUS	5	74.02404	MW	20.81969	MVAR	
T0-BUS	2	65.22739	MW	43.43988	MVAR	
2	0.9800	-1.49	135.00000	31.11910	75.00000	60.00000
T0-BUS	5	46.91624	MW	-2.89952	MVAR	
T0-BUS	3	76.71990	MW	53.11388	MVAR	
T0-BUS	1	-63.63718	MW	-79.09526	MVAR	
3	0.9340	-3.94	0.00000	0.00000	60.00000	50.00000
T0-BUS	4	16.72826	MW	-1.58446	MVAR	
T0-BUS	2	-76.71990	MW	-48.39773	MVAR	
4	0.9068	-5.25	0.00000	0.00000	70.00000	55.00000
T0-BUS	5	-53.51378	MW	-31.88358	MVAR	
T0-BUS	3	-16.49206	MW	-23.12670	MVAR	
5	0.9727	-2.58	0.00000	0.00000	65.00000	45.00000
T0-BUS	1	-71.84075	MW	-65.17135	MVAR	
T0-BUS	2	-46.68237	MW	-15.22950	MVAR	
T0-BUS	4	53.51378	MW	35.36267	MVAR	

Figure 8: Power Flow — Part 4

1	1	(9.109589,	-25.508904)
2	2	(10.882353,	-57.452787)
3	3	(2.000000,	-25.850000)
4	4	(2.000000,	-19.413368)
5	5	(9.991942,	-46.638316)
5	1	(-4.109589,	10.958904)
1	5	(-4.109589,	10.958904)
2	1	(-5.000000,	15.000000)
1	2	(-5.000000,	15.000000)
5	2	(-5.882353,	23.529412)
2	5	(-5.882353,	23.529412)
4	3	(-2.000000,	6.000000)
3	4	(-2.000000,	6.000000)
5	4	(0.000000,	13.020833)
4	5	(0.000000,	13.020833)
3	2	(0.000000,	19.607843)
2	3	(0.000000,	19.607843)

Figure 9: Y_{Bus} — Part 4

2.5 Part 5

Experimentally, we tweak the values of the real power load to find the point at which the power flow diverges. When changing by 50[MW], we see that this occurs at 420[MW]. Changing values slightly, we observe that the power flow diverges for $P_L \geq 409$ [MW]

2.6 Part 6

Now modifying to the power constraints for bus 2, as specified in Part (2), we find that the power flow diverges for $P_L \geq 388$ [MW].

2.7 Part 7

For the power flow to not diverge, we need at least .34[p.u.] shunt capacitance. We slowly increase this value to find that, to maintain a bus voltage greater than .9[p.u.] at a 400[MW] real load, with power constraints from Part (2), the shunt capacitance must be at least 1.51[p.u.].

3 Analysis

3.1 Constructing Y_{bus}

We may begin by constructing an admittance matrix based on the provided parameters. First and foremost, we may determine the zero parameters based on disconnected buses:

$$Y_{bus} = \begin{bmatrix} - & - & 0 & 0 & - \\ - & - & - & 0 & - \\ 0 & - & - & - & 0 \\ 0 & 0 & - & - & - \\ - & - & 0 & - & - \end{bmatrix}$$

From here, we find the off-diagonal elements by taking the inverse of the impedance. This gives us:

$$y_{12} = y_{21} = -\frac{1}{.02 + .06j} = -5 + 15j$$

$$y_{15} = y_{51} = -\frac{1}{.03 + .08j} = -4.1096 + 10.9589j$$

$$y_{23} = y_{32} = -\frac{1}{(.92)(.05j)} = 21.739j$$

$$y_{25} = y_{52} = -\frac{1}{.01 + .04j} = -5.8824 + 23.5294j$$

$$y_{34} = y_{43} = -\frac{1}{.05 + .15j} = -2 + 6j$$

$$y_{45} = y_{54} = -\frac{1}{(.96)(.08j)} = 13.021j$$

Putting this into our matrix, we get:

$$Y_{bus} = \begin{bmatrix} - & -5 + 15j & 0 & 0 & -4.1096 + 10.9589j \\ -5 + 15j & - & 21.739j & 0 & -5.8824 + 23.5294j \\ 0 & 21.739j & - & -2 + 6j & 0 \\ 0 & 0 & -2 + 6j & - & 13.021j \\ -4.1096 + 10.9589j & -5.8824 + 23.5294j & 0 & 13.021j & - \end{bmatrix}$$

Finally, we determine the diagonal terms:

$$y_{11} = -y_{12} - y_{15} + \frac{(B_{12} + B_{15})j}{2} = 9.0196 - 25.5089j$$

Using a similar method, we get:

$$y_{22} = 10.882 - 61.859j$$

$$y_{33} = 2 - 25.85j$$

$$y_{44} = 2 - 19.413j$$

$$y_{55} = 9.992 - 46.638j$$

This gives us the final bus matrix (for parts 1 and 2) as:

$$\begin{bmatrix} 9.0196 - 25.5089j & -5 + 15j & 0 & 0 & -4.1096 + 10.9589j \\ -5 + 15j & 10.882 - 61.859j & 21.739j & 0 & -5.8824 + 23.5294j \\ 0 & 21.739j & 2 - 25.85j & -2 + 6j & 0 \\ 0 & 0 & -2 + 6j & 2 - 19.413j & 13.021j \\ -4.1096 + 10.9589j & -5.8824 + 23.5294j & 0 & 13.021j & 9.992 - 46.638j \end{bmatrix}$$

We may observe that this is in line with the generated buses from the results section.

With the connection of the shunt capacitor in part (3), we modify the bus to get:

$$\begin{bmatrix} 9.0196 - 25.5089j & -5 + 15j & 0 & 0 & -4.1096 + 10.9589j \\ -5 + 15j & 10.882 - 61.859j & 21.739j & 0 & -5.8824 + 23.5294j \\ 0 & 21.739j & 2 - 25.65j & -2 + 6j & 0 \\ 0 & 0 & -2 + 6j & 2 - 19.413j & 13.021j \\ -4.1096 + 10.9589j & -5.8824 + 23.5294j & 0 & 13.021j & 9.992 - 46.638j \end{bmatrix}$$

Finally, changing the tap in part (4) would result in:

$$\begin{bmatrix} 9.0196 - 25.5089j & -5 + 15j & 0 & 0 & -4.1096 + 10.9589j \\ -5 + 15j & 10.882 - 57.453j & 19.608j & 0 & -5.8824 + 23.5294j \\ 0 & 19.608j & 2 - 25.65j & -2 + 6j & 0 \\ 0 & 0 & -2 + 6j & 2 - 19.413j & 13.021j \\ -4.1096 + 10.9589j & -5.8824 + 23.5294j & 0 & 13.021j & 9.992 - 46.638j \end{bmatrix}$$

We may see that the constructed buses match those generated in PET, with small variations due to rounding.

3.2 Conclusions

First and foremost, we may see that the admittance matrix simulated is precisely as expected. From parts one to two, there is no difference since no new components are connected. For part three, the addition of a shunt capacitor causes a shift in bus 3's diagonal term. For part 4, the change in the tap value of the transform causes a change in bus 2 and bus 3's values.

For the power flow, we may observe that, transitioning from part one to two, as expected, the generator from bus 1 must pick up the slack caused by stricter limitations on bus 2's reactive power flow. Furthermore, as expected, we may see that the addition of a shunt capacitor in part 3 changes very little for the real power flow; however, the reactive power flow to bus 3 decreases, while it increases for the other buses. Conversely, the increase of the tap in part 4 results in decreased real power flow to bus 3, while the real power flow to other buses increases (with little change in reactive power flow). As such, we see that the PET program does a great job of simulating bus responses to changes in power flow set up.

3.3 Voltage Magnitude versus Real Power Load

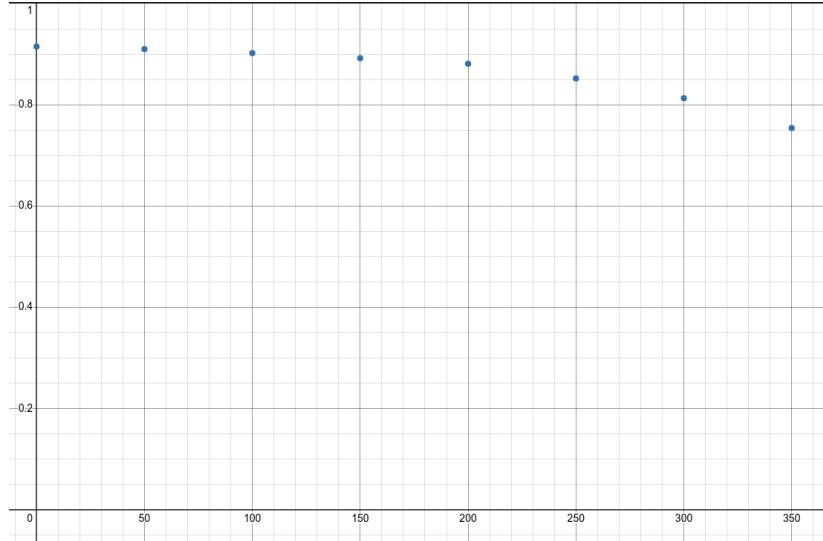


Figure 10: Plot for Part 5

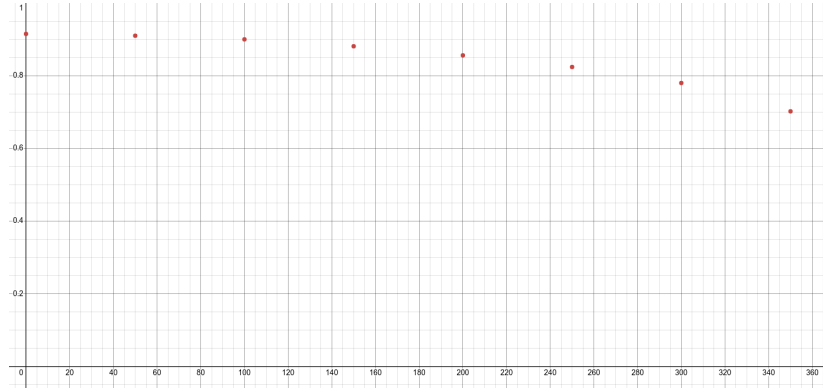


Figure 11: Plot for Part 6

Based on the PV plots, we may determine that the voltage is inversely related to the real power load, while reactive power load stays constant. This is the reason that reactive power injection is desirable, as it allows for voltage magnitude to remain more steady.

3.4 How to Determine the Necessary Capacitance for Part 7

Using the set up of the problem, we could simulate using the Newton-Raphsson method to determine the necessary capacitance value.

3.5 Converting the Capacitance to Farads

Given the base, we know that the capacitor base impedance is:

$$X_b = \frac{V^2}{Q}$$

$$X_b = \frac{(34.5 \cdot 10^3)^2}{100 \cdot 10^6 \sin(60)j}$$

$$X_b = -13.744j[\Omega]$$

We know that capacitance may be written as:

$$X_C = \frac{1}{j\omega C}$$

This means:

$$\frac{1}{\omega C} = 13.744$$

$$C = \frac{1}{13.744\omega}$$

$$C = \frac{1}{13.744(120\pi)}$$

$$C_b = 193[\mu\text{F}]$$

Now that we know the base in farads, we may simply multiply by the per-unit value to get:

$$C = C_b C_{pu}$$

$$C = (1.51)(193 \cdot 10^{-6})$$

$$\boxed{C = 291[\mu\text{F}]}$$