

# Homework 1

Michael Brodskiy

Professor: A. Abur

September 20, 2024

## Chapter 2:

4. First, we find the angle difference,  $\phi$ :

$$\phi_1 = \cos^{-1}(.707)$$

$$\phi_1 \approx 45^\circ$$

From here, we find the initial load current, based on the provided load voltage and power draw:

$$V_L = 440 \text{ [V]}$$

$$\hat{I}_L = \frac{200 \cdot 10^3}{\sqrt{3}(44)(.707)} \angle -\phi_1$$

$$\hat{I}_L = 371.19 \angle -45^\circ$$

We know that power may be expressed as:

$$S = P + jQ$$

We find the reactive power of the load:

$$Q = P \frac{\sin(\phi_1)}{\cos(\phi_1)} = P \tan(\phi_1)$$

$$Q = 200 \text{ [kVAr]}$$

Adding the capacitors in parallel allows us to sum the net positive VArS:

$$Q_{net} = 200 - 50 = 150 \text{ [kVAr]}$$

The new power factor becomes:

$$\phi_2 = \tan^{-1} \left( \frac{150[\text{kVAr}]}{200[\text{kW}]} \right) = \tan^{-1}(.75) = 36.87^\circ$$

$$pf_2 = \cos(36.87) = .8 \text{ lagging}$$

The current then becomes:

$$I_{L2} = \frac{200 \cdot 10^3}{\sqrt{3}(440)(.8)} = 328.04$$

$$\hat{I}_{L2} = 328.04 \angle -36.87^\circ$$

5. (a) We begin by finding the reactive component of the load:

$$Q = P \tan(\cos^{-1}(pf)) = 10 \tan(\cos^{-1}(.9))$$

$$Q = 4.843[\text{kVAr}]$$

Putting the components together, we get:

$$S = P + jQ$$

$$S = 10 + 4.843j[\text{V A}]$$

- (b) To find the magnitude of the current, we may use the following relation:

$$P = IV(pf)$$

We insert known values:

$$10^4 = (I)(416)(.9)$$

This gives us:

$$|I| = \frac{10^4}{416(.9)}$$

$$|I| = 26.709[\text{A}]$$

- (c) Assuming  $\angle I = 0$ , we can say:

$$\hat{I} = 26.709 \angle 0^\circ [\text{A}]$$

And from this we say:

$$\hat{V} = 416 \angle \cos^{-1}(.9)$$

$$\hat{V} = 416\angle 25.84^\circ [\text{V}]$$

We multiply the two together to find the power:

$$p(t) = \hat{I}\hat{V} = 26.709\angle 0^\circ \cdot 416\angle 25.84^\circ$$

$$p(t) = 11.111\angle 25.84^\circ [\text{kW}]$$

11. The first step has us converting  $\Delta$  connections to ‘Y’ connections:

$$Z_Y = -\frac{Z_\Delta}{3} = -\frac{1}{3}j[\Omega]$$

$$\hat{V}_{a''n} = \frac{\sqrt{3}}{3}\hat{V}_{ab''}\angle -30^\circ = \frac{\sqrt{3}}{3}\angle -30^\circ [\text{V}]$$

We may then find values for all of the voltages (only the angles change):

$$\begin{bmatrix} V_{a''n} \\ V_{b''n} \\ V_{c''n} \end{bmatrix} = \frac{\sqrt{3}}{3}\angle \begin{bmatrix} -30 \\ -150 \\ 90 \end{bmatrix}^\circ [\text{V}]$$

Using equivalence, we can develop a single-phase circuit as follows:

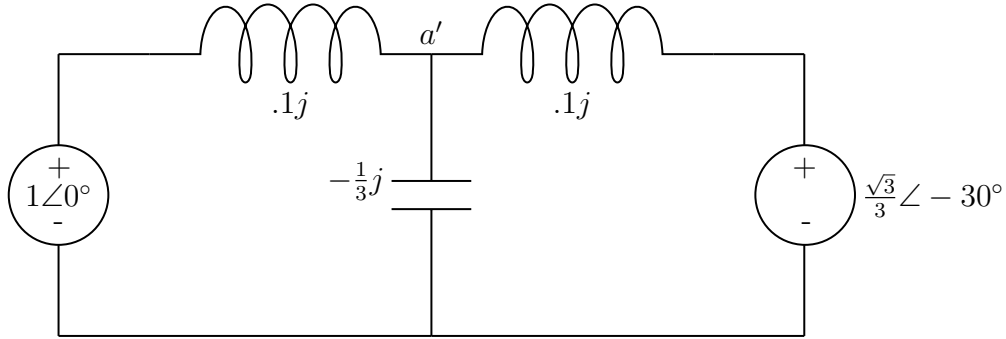


Figure 1: Single Phase Equivalent Circuit

We can write equations using the voltages at  $a'$ :

$$\frac{V_{an} - V_{a'n}}{.1j} + \frac{V_{a''n} - V_{a'n}}{.1j} + \frac{3V_{a'n}}{j} = 0$$

We move  $V_{a'n}$  to one side:

$$\frac{17V_{a'n}}{j} = \frac{10V_{an}}{j} + \frac{10V_{a''n}}{j}$$

$$\begin{aligned}
V_{a'n} &= \frac{10(V_{an} + V_{a''n})}{17} \\
V_{a'n} &= \frac{10(1 + .5 - .2887j)}{17} \\
V_{a'n} &= \frac{15 - 2.887j}{17} \\
V_{a'n} &= .8824 - .1698j
\end{aligned}$$

Converting back to phasor form, we find:

$$\hat{V}_{a'n} = .8986 \angle -10.9^\circ [\text{V}]$$

Given that the rest of the voltages are offset by  $120^\circ$ , we may write:

$$\boxed{\begin{bmatrix} V_{a'n} \\ V_{b'n} \\ V_{c'n} \end{bmatrix} = .8986 \angle \begin{bmatrix} -10.9 \\ -130.9 \\ 109.1 \end{bmatrix}^\circ [\text{V}]}$$

From here, we finally find  $V_{a'b'}$  since we know this is the difference between  $V_{a'n}$  and  $V_{b'n}$ :

$$\begin{aligned}
V_{a'b'} &= V_{a'n} - V_{b'n} \\
V_{a'b'} &= .8986 (\angle -10.9^\circ - \angle -130.9^\circ) \\
V_{a'b'} &= .8986 [(.982 - .1891j) - (-.6547 - .7559j)] \\
V_{a'b'} &= .8986 [1.6367 + .5668j] \\
V_{a'b'} &= 1.4707 + .5093j
\end{aligned}$$

And finally we convert to phasor form:

$$\boxed{\hat{V}_{a'b'} = 1.5564 \angle 19.1^\circ [\text{V}]}$$

12. We begin by, as always, converting to a ‘Y’ configuration:

$$Z_C \rightarrow \frac{Z_C}{3} = -\frac{10}{3}j[\Omega]$$

This leads to a parallel combination, the equivalent impedance of which we may calculate:

$$Z_{eq} = \frac{-(10/3)(10)}{10 - (10/3)}j = -5j[\Omega]$$

The circuit can then be phase-simplified by drawing:

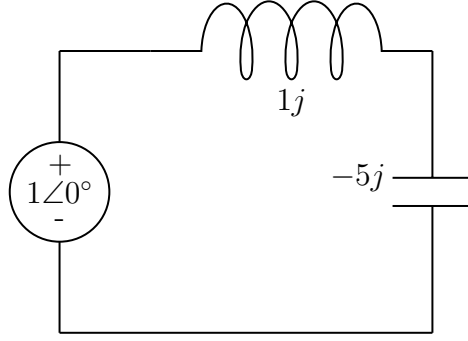


Figure 2: Single Phase Equivalent Circuit

Summing impedances, the total becomes:

$$Z_t = -4j[\Omega]$$

The line current can then be calculated as:

$$I_a = \frac{1}{-4j}$$

$$\hat{I}_a = \frac{(1\angle 0^\circ)j}{4}$$

$$\hat{I}_a = .25\angle 90^\circ[\text{A}]$$

To find the current through a capacitor, we must find the voltage across one of load phase components:

$$V_{pha} = (-5j)(.25\angle 90^\circ)$$

$$V_{pha} = (-5j)(.25j)$$

$$\hat{V}_{pha} = 1.25\angle 0^\circ[\text{V}]$$

Because of the parallel nature of the capacitor-inductor network, this voltage flows into both branches. To find the current across one capacitor, we find:

$$I_{cap} = \frac{(\sqrt{3})1.25\angle 0^\circ}{-10j}$$

$$I_{cap} = \frac{(\sqrt{3})1.25j}{10}$$

$$I_{cap} = .2165j$$

$$\boxed{I_{cap} = .2165 \angle 90^\circ [\text{A}]}$$

The complex power of the load may be calculated by using the product of the voltage and current phasors. This gives us:

$$S = 3|\hat{V}||\hat{I}|$$

$$S = 3(1.25)(.25)$$

$$\boxed{S = .9375 [\text{V A}]}$$