

Lab Two  
Power Systems Analysis  
EECE5682

Michael BRODSKIY  
Brodskiy.M@Northeastern.edu

October 3, 2024

Date Performed: September 28, 2024  
Instructor: Professor ABUR

### **Abstract**

This laboratory experiment explores three-phase circuit modeling via SimuLink integration into MATLAB. The experiment simulates a provided circuit design and demonstrates the applicability of single-phase equivalence modeling for balanced three-phase circuits.

KEYWORDS: three-phase, modeling, SimuLink, MATLAB, single-phase equivalence, balanced

## 1 Introduction & Objectives

This experiment begins by integrating the following diagram into MATLAB's SimuLink environment:

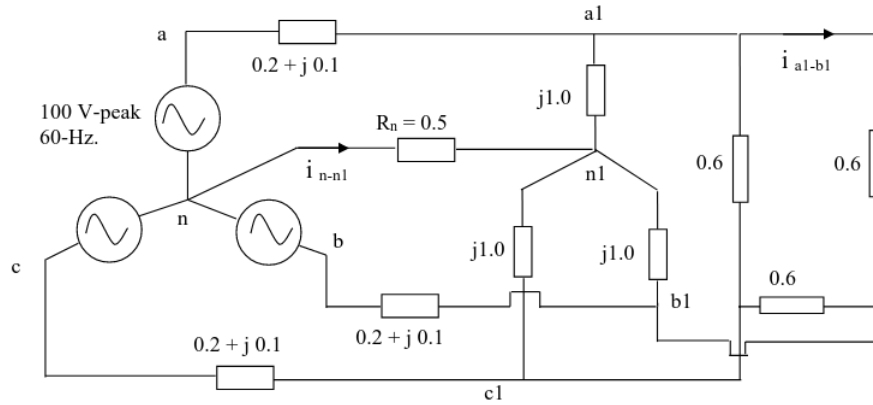


Figure 1: Simulated Circuit

After simulating the circuit, data related to the voltage at various nodes and current through various loops was taken, most importantly nodes  $a_1$  to  $b_1$ , and along the neutral line  $n_1$  to  $n$ .

## 2 Results & Analysis

### 2.1 Original Circuit

The first step of the experiment is to plot the waveforms of  $V_{a_1 \rightarrow b_1}$ ,  $I_{a_1 \rightarrow b_1}$ , and  $I_{n \rightarrow n_1}$ . The result is shown in Figure 2 below:

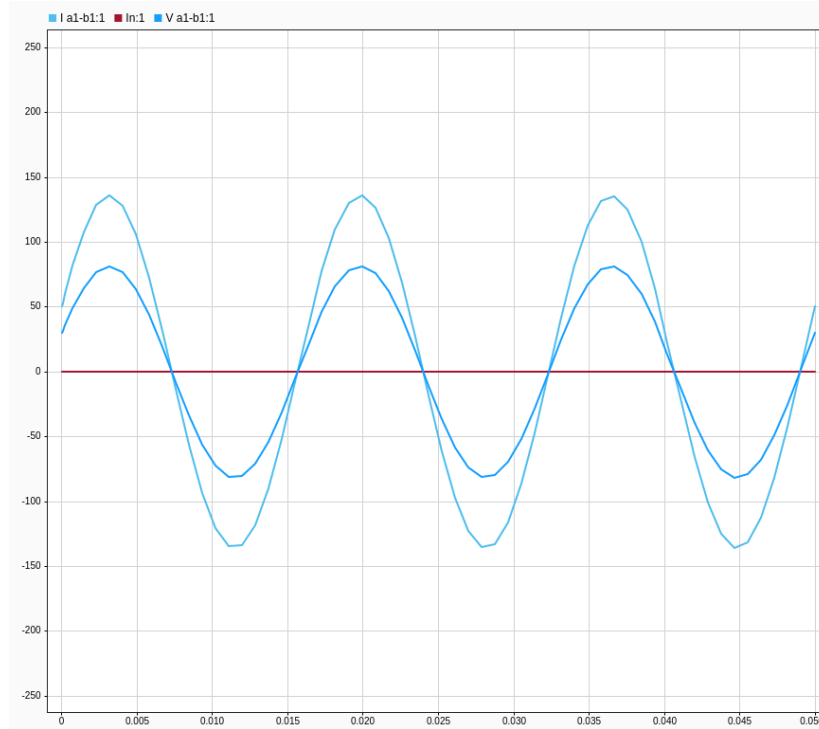


Figure 2: Waveforms for Part (a)

Here, we see the waveforms. Note that the neutral line has no current, as would be expected for a balanced circuit. From here, we construct a single phase equivalent circuit using Phase  $a$ . The circuit becomes:

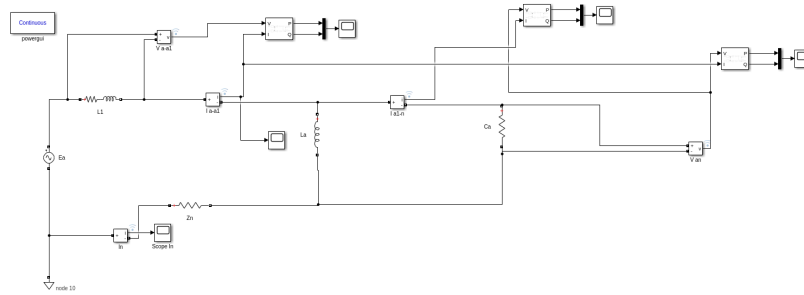


Figure 3: Single Phase Equivalent Circuit (Phase  $a$ )

Note that for the equivalent circuit,  $C_a = .2[\Omega]$  instead of the original  $.6$ , since the configuration was in delta instead of 'Y' form.

## 2.2 Modified Circuit

Using the circuit to simulate, we may obtain the equivalent waveforms for  $V_{a_1 \rightarrow b_1}$  and  $I_{a_1 \rightarrow b_1}$ :

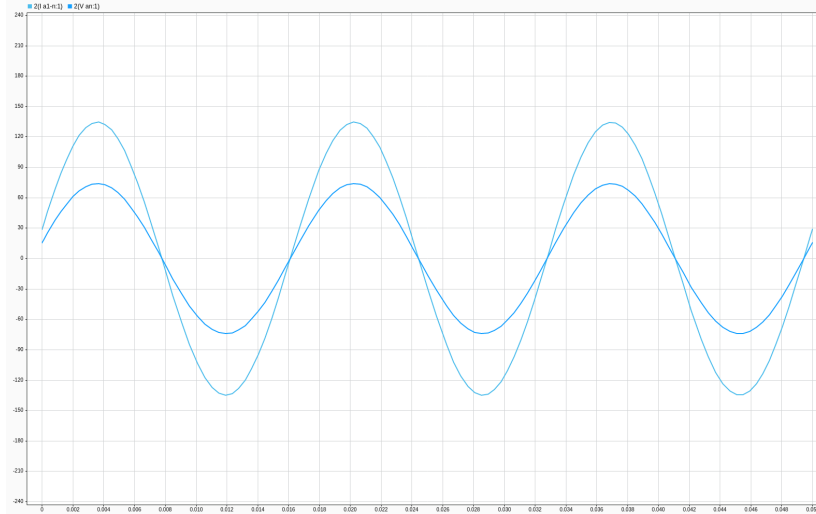


Figure 4: Waveforms Plotted Using Single-Phase Equivalent

Note that, as expected, the waveforms are equivalent to those shown in Figure 2

## 2.3 Changing the Neutral Line Impedance

From here, we return to the original three-phase circuit, but now we modify the parameters. First, we change the neutral line impedance from  $R_n = .5[\Omega]$  to  $R_n = 50[\Omega]$ . Plotting the same waveforms, we get:

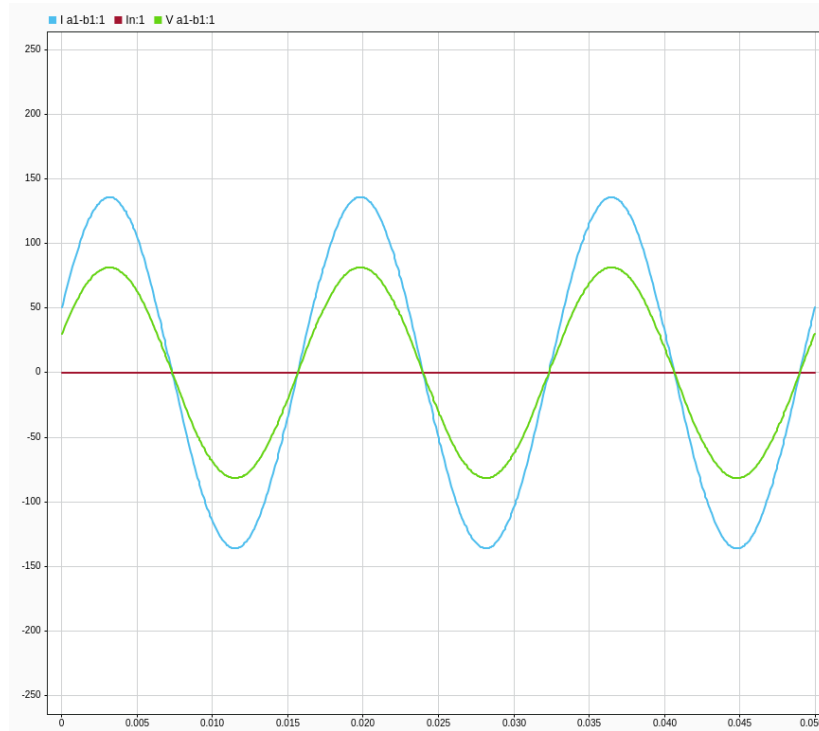


Figure 5: Waveforms with Changed Neutral Line Impedance

Once again, we see no change, as expected. This is because the neutral line still experiences no current flow, as the circuit remains balanced.

## 2.4 Unbalancing the Circuit

We now change the impedance from  $a_1$  to  $n_1$  by a factor of ten. This results in the following waveforms:

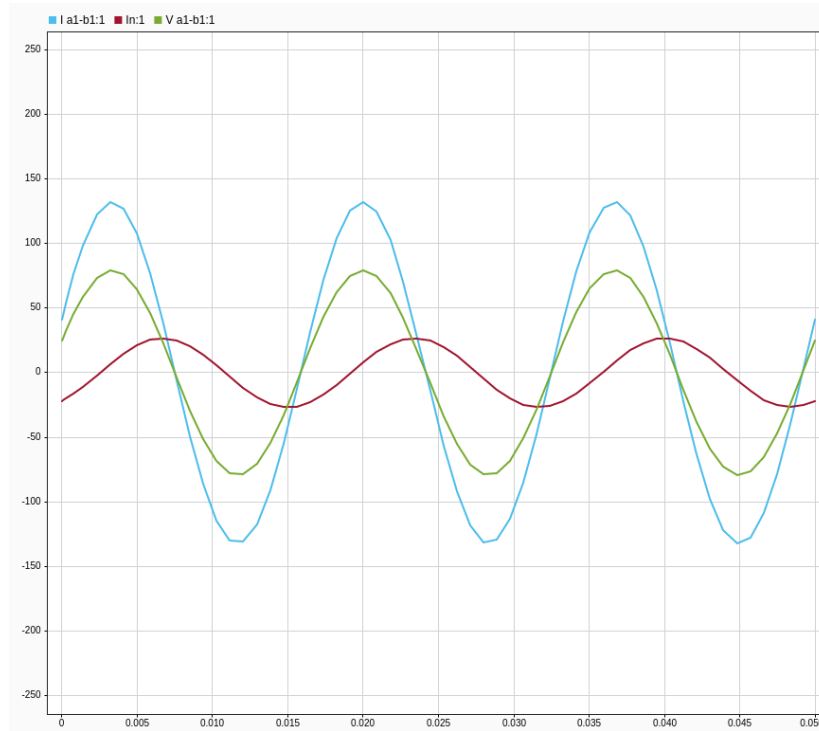


Figure 6: Waveforms for the Now-Unbalanced Circuit

We may notice with this waveform that, although the line-to-line difference remains the same, there is now a line-to-neutral difference. This causes current to flow through the neutral line, which can be seen by the red line.

### 3 Conclusion

Throughout this experiment, we verified several important concepts related to three-phase circuits. Namely, we confirmed that, for balanced three-phase circuits, a single-phase equivalent may be used to analyze each phase more easily. Additionally, we confirmed that current flows through the neutral line only in the unbalanced case.