

Lecture 7

Michael Brodskiy

Professor: A. Ali

September 30, 2024

- Generator Model

- Synchronous Generator

- * Consists of a rotor (rotating piece)
 - * And a stator
 - * Rotating part consists of a coil receiving D.C. current, with a magnetic orientation
 - * The rotation results in a flux, which passes through the stator
 - * From this, we can obtain (with $\lambda = N\phi$):

$$\frac{d\lambda}{dt} = e = \omega k \sin(\omega t)$$

$$|\hat{E}_f| = 4.44fN\phi_{max} \propto I_{dc}, \omega$$

$$\lambda = k \cos(\omega t)$$

- * The terminal voltage may be written as:

$$\hat{V}_t = \hat{E}_f - (r + jX_s)\hat{I}_a$$

- * We see that terminal voltage may be controlled using \hat{E}_f
 - * The net injected current at different buses (substations) may be calculated using:

$$\hat{I}_i = \frac{(P_{Gi} + jQ_{Gi})^*}{\hat{V}_i^*}$$

- * For buses without a generator, there is no source injection or load, so there is no net current injection (zero-injection bus)
 - Such substations may be used as 'switching' substations

- Transmission Lines

- For a transmission line with resistance r and impedance jx , we add two capacitors, one on each side of the impedance, with value jb
- With this model, we may write:

$$jb = \frac{1}{2}jb_{lc}$$

- * Where b_{lc} is the total line charging susceptance of the line
- At a bus with a load, we may find the current as:

$$\hat{I}_2 = \frac{(\hat{V}_2 - \hat{V}_1)}{r_{12} + jx_{12}} + \hat{V}_2jb_{12} + \frac{(\hat{V}_2 - \hat{V}_3)}{r_{23} + jx_{23}} + \hat{V}_2jb_{23} + \frac{(\hat{V}_2 - \hat{V}_4)}{r_{24} + jx_{24}} + \hat{V}_2jb_{24} +$$

- Bus Admittance Matrix

- We may build a bus admittance matrix (Y_{bus}) may be built by inspection:

$$Y_{bus}(i, i) = \text{sum of admittances of all branches incident to bus } i$$

$$Y_{bus}(i, j) = \text{negative of the admittance of the branch connecting bus } i \text{ and } j$$

$$Y_{bus}(i, j) = Y_{bus}(j, i)$$

- Properties of Y_{bus} :

- * Symmetric square matrix
- * Has complex entries
- * Super sparse (*i.e.* majority of the entries are zero)
- * Y_{bus} is non-singular only if there exists at least one branch connecting a bus to ground
- * $(Y_{bus})^{-1} = Z_{bus}$ — the bus impedance matrix!

- Properties of Z_{bus} :

- * It is a full matrix
- * It is a symmetric matrix
- * Diagonal entries are equal to the Thévenin equivalent impedances looking into the network at that bus
 - This means Thévenin equivalents may be formulated by finding Z_{bus} and finding the corresponding diagonal entry for a bus